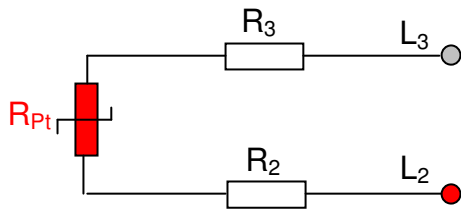


# The effect of 2, 3 or 4 wire connection using Pt100/RTDs


## 2-wire connection



$$R_{Pt\ 100} = R_{Pt} + R_2 + R_3$$

The wire resistances  $R_2$  and  $R_3$  are inevitably included in the measured value. Wire resistance can be cancelled by calibration, but just at one specific temperature of the wire (often room temperature).

## 3-wire connection

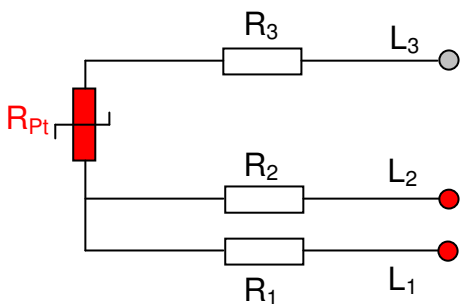


$$\Omega_1 = R_2 + R_{Pt} + R_3$$

$$\Omega_2 = R_1 + R_2$$

$$\Omega_1 - \Omega_2 = R_{Pt\ 100} = R_{Pt} + R_3 - R_1$$

If and only if the wire resistances  $R_1$  and  $R_3$  are equal you measure the true Pt100 resistance. As the wire  $L_2$  also is coloured red (and hard to follow) you have to keep all the wire resistances  $R_1$ ,  $R_2$  and  $R_3$  equal.

## 4-wire connection

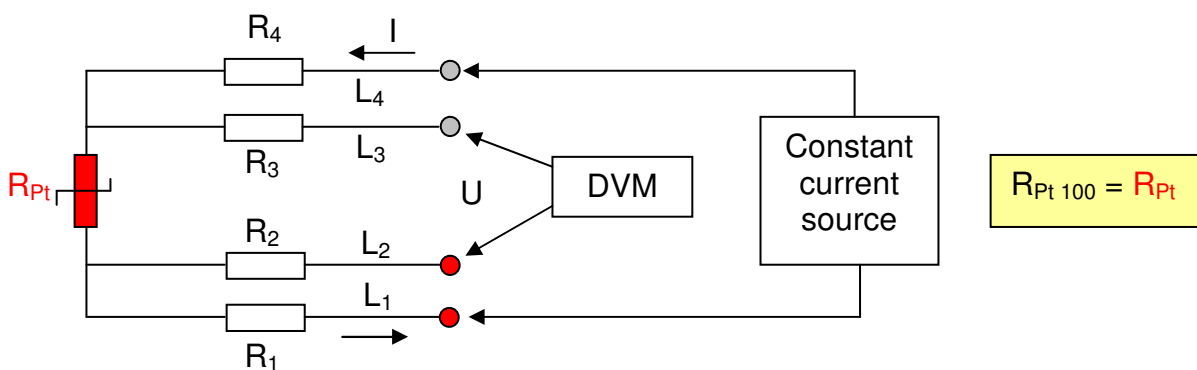

$$R_{Pt\ 100} = R_{Pt}$$

The current source will maintain the excitation current constantly (0,1 – 1 mA). Following the Law of Ohm,  $R = U / I$ , the resistance can be calculated. The digital voltmeter, DVM, has an input impedance of at least 10 Mohms. Thus just an extremely small current will pass through the DVM which means that the voltage drops over the wire resistances  $R_2$  and  $R_3$  will be practically none.